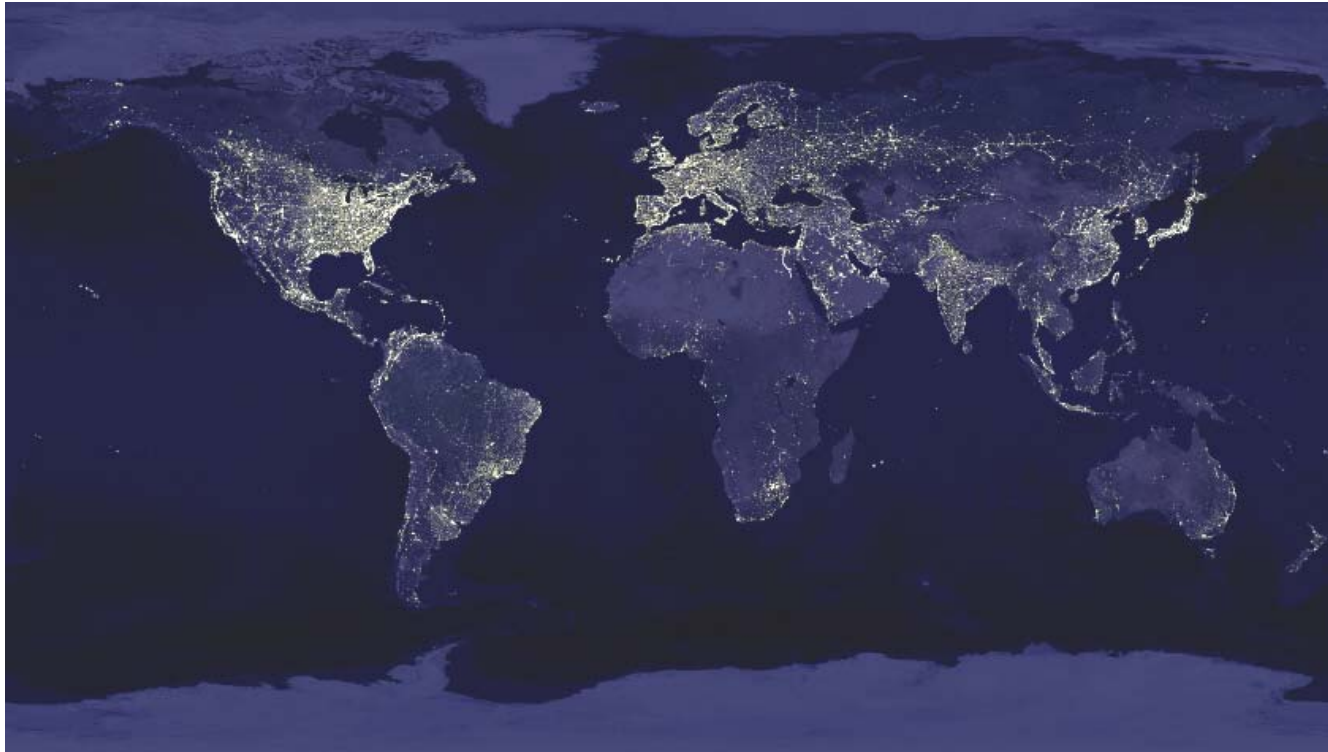





Custom Green Voltage Regulators for Portable Electronics




Old Fashioned LED Driver

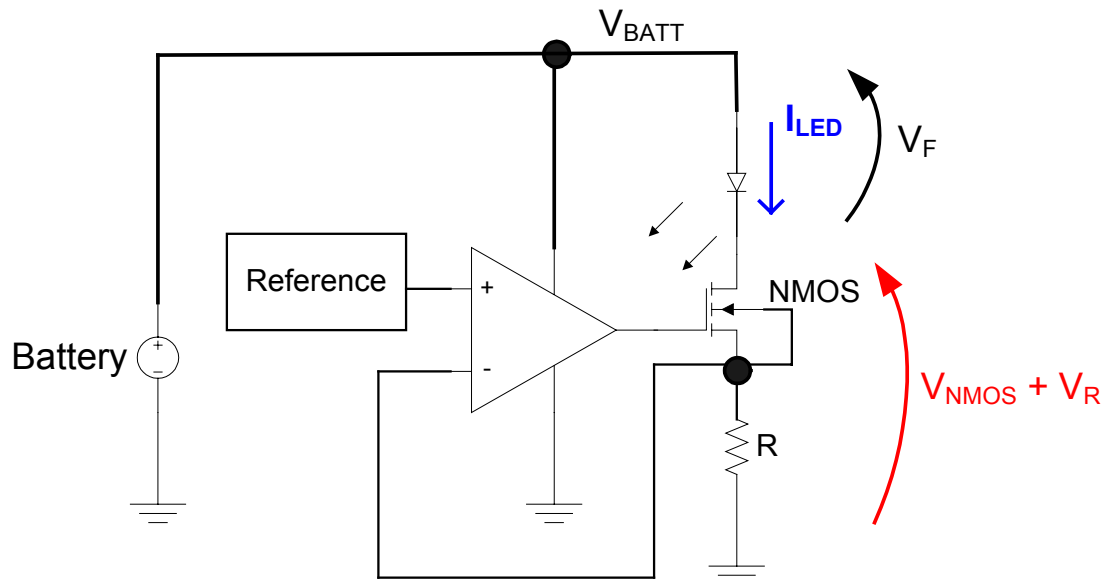- ◆ LED Forward Voltage V_F depends on the current
- ◆ Minimum Voltage of V_{BATT} is: $V_F + V_{NMOS} + V_R$
- ◆ Wasted Power is: $I_{LED} * (V_{NMOS} + V_R)$
 - Ignoring power loss in the Reference and Op Amp




Linear (or LDO) LED Driver

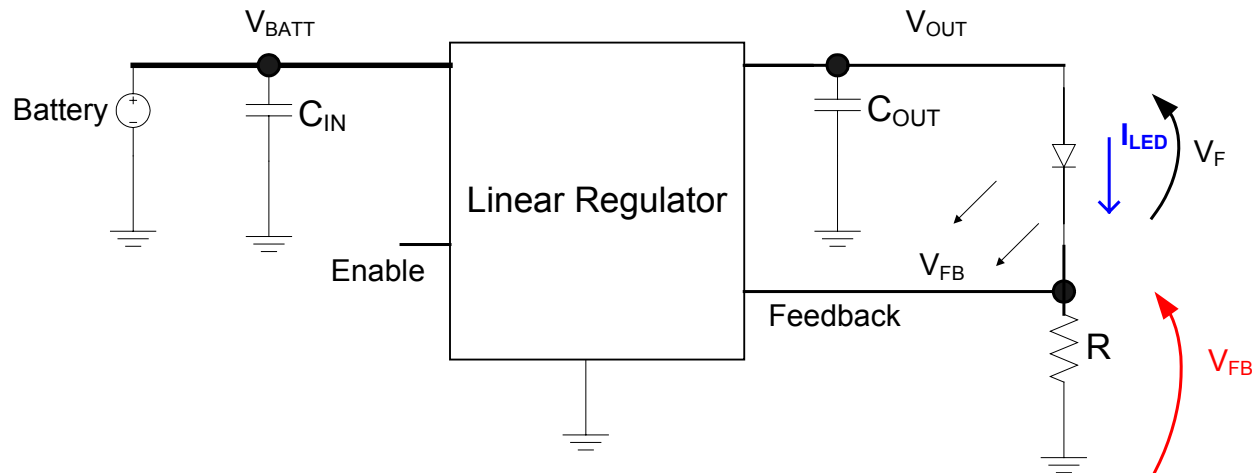- ◆ LED Forward Voltage V_F depends on the current
- ◆ Minimum Voltage of V_{BATT} is roughly $V_F + V_{FB}$
- ◆ Wasted Power is: $I_{LED} * [(V_{FB}) + (V_{BATT} - V_{OUT})]$
- ◆ Lowering the value of V_F
 - Will NOT save any power
 - Improves Operating Range



Using Step-Down (Buck) Regulator


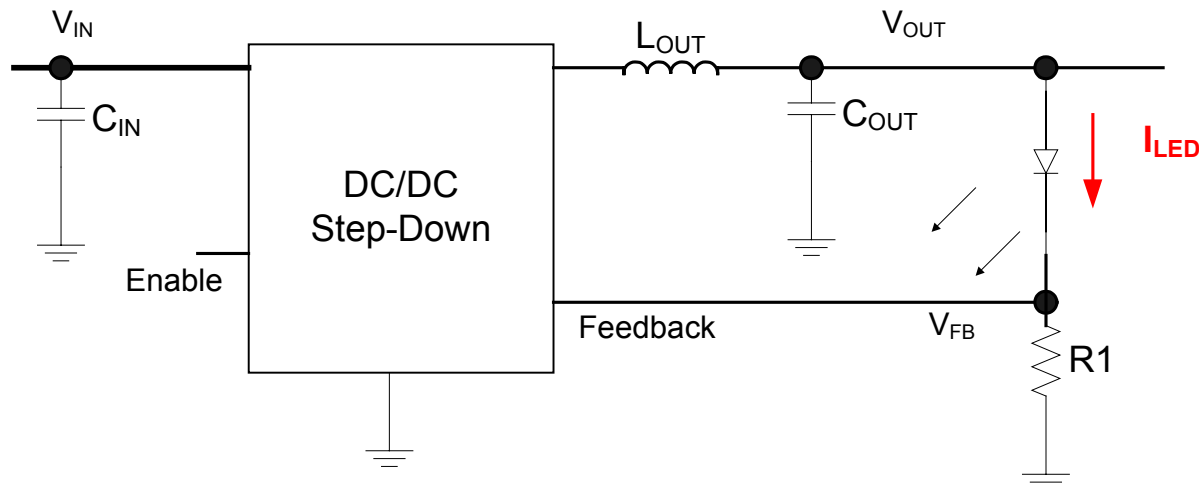
- ◆ Minimum Voltage of V_{BATT} is roughly $V_F + V_{FB}$
- ◆ Wasted Power is: $I_{LED} * (V_{FB}) + P_{DC/DC}$
- ◆ Lowering the value of V_F
 - WILL save power
 - Improves operating range



Li-Polymer Range vs. Feedback

◆ Buck LED Driver With 100% Duty Cycle

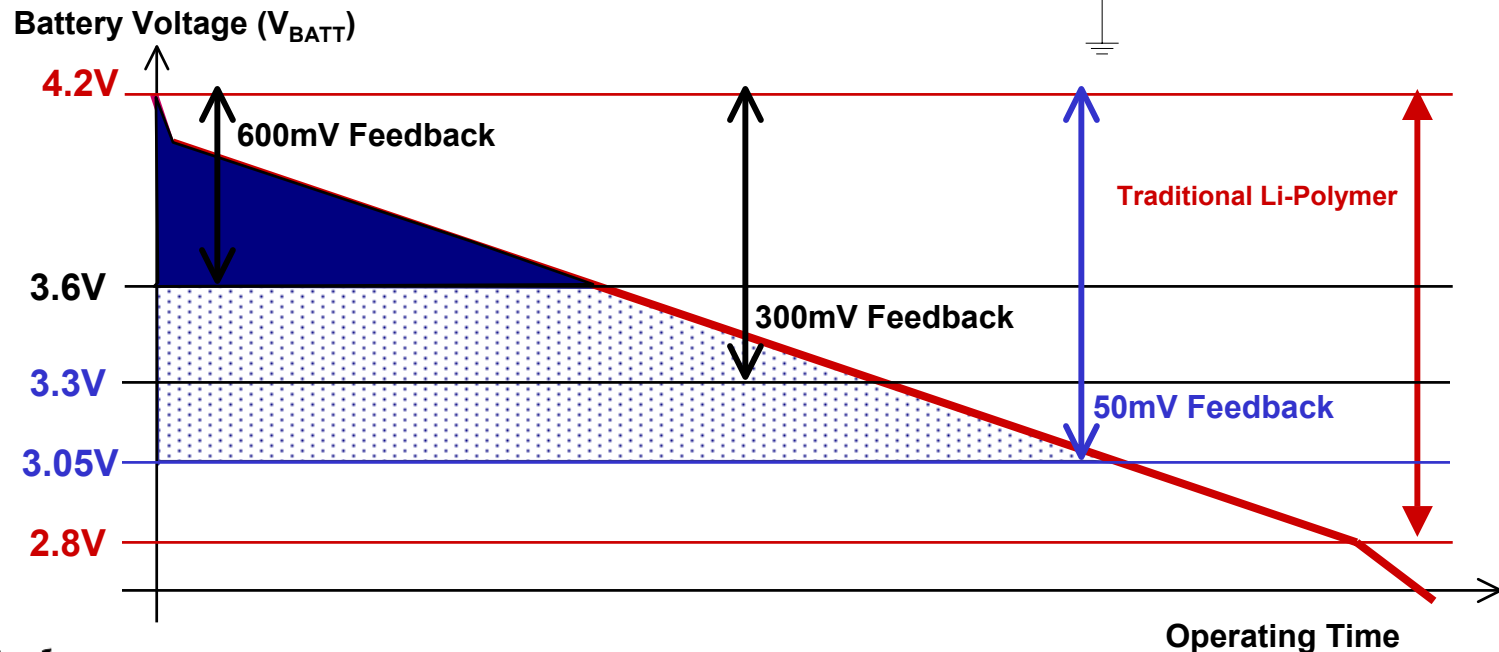
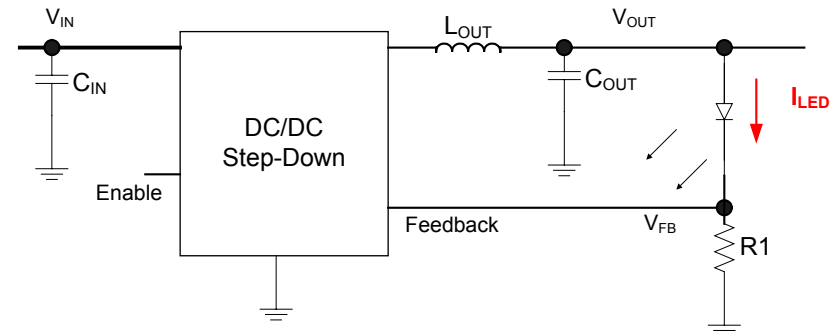
- LED @ 350mA with $V_F = 3V$
- V_{FB} of 600mV, 300mV and 50mV



Operating Time Vs. Feedback Voltage



◆ Circuit Using A Step-Down DC/DC

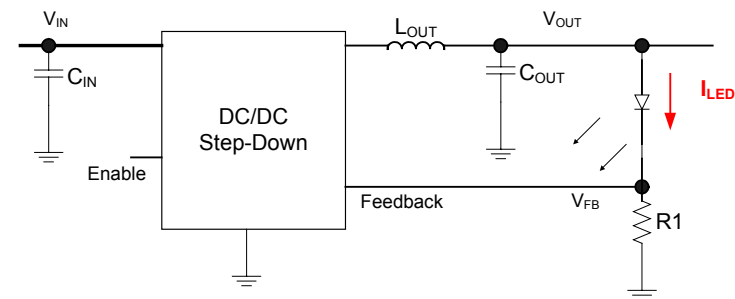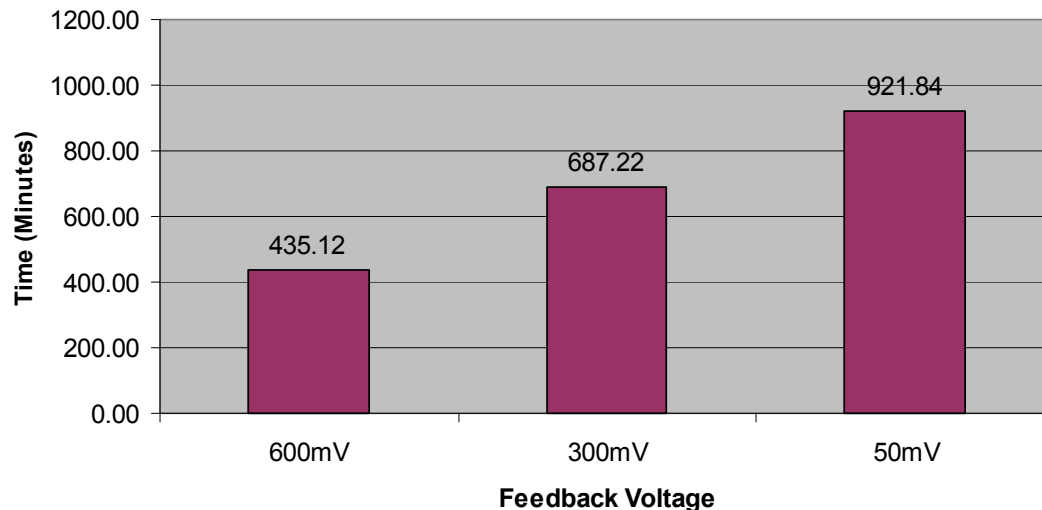- Battery Is Assumed To Be 5000mAHr
- 90% Efficiency For the DC/DC Regulator
- Input Is Assumed To Be One Li-Polymer Battery (4.2V to 3V)
- $I_{LED}=350mA$ & Forward Voltage of 3V (1 Watt LED Power)
- Feedback Voltages (V_{FB}) of 600mV, 300mV and 50mV



Operating Time Vs. Feedback Voltage

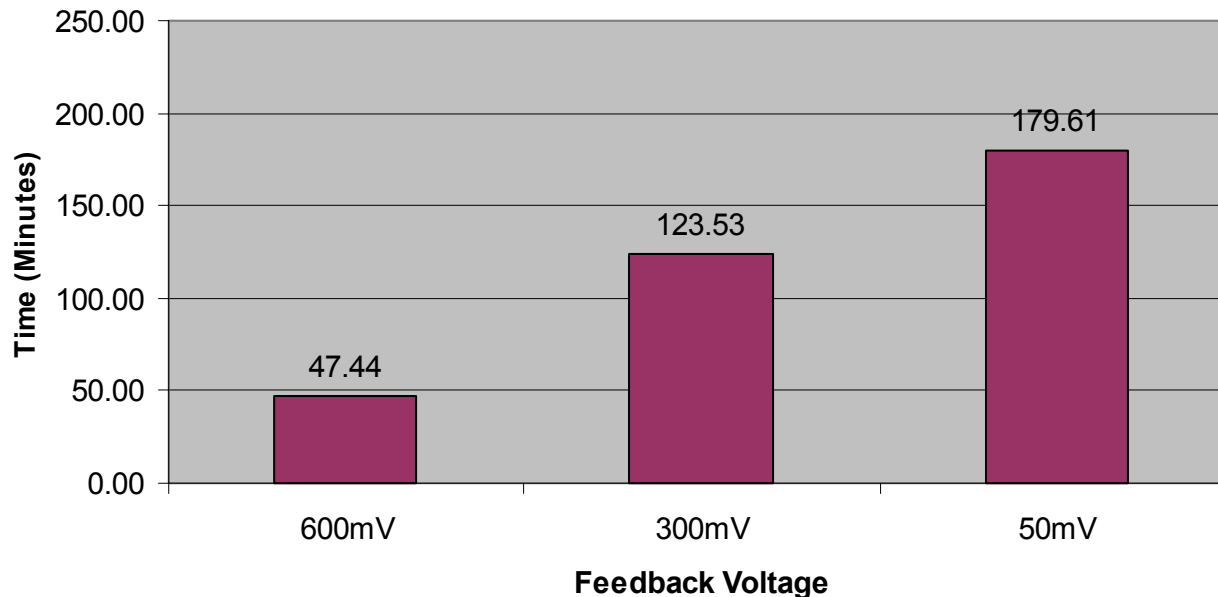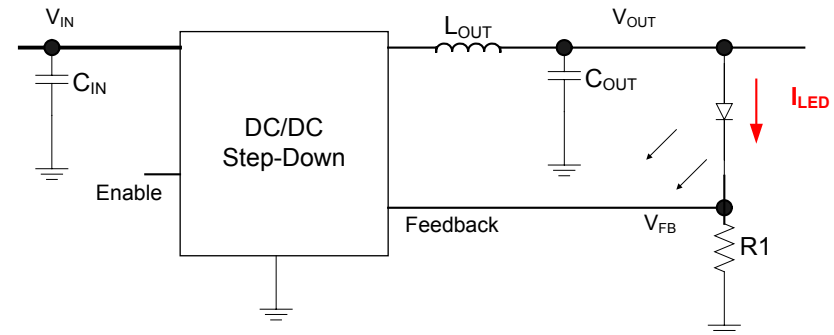- ◆ Buck LED Driver
 - V_{FB} of 600mV, 300mV and 50mV
- ◆ One LED
 - 600mA @ $V_F = 3.4V$
- ◆ One Li-Polymer (1600mAHr)
 - Cut-off @ 3.45V




Operating Time vs. LED Forward Voltage

◆ LED @ 350mA

■ Linear Solution vs. DC/DC

- Black: Linear
- Red: $V_{FB} = 600\text{mV}$
- Blue: $V_{FB} = 50\text{mV}$

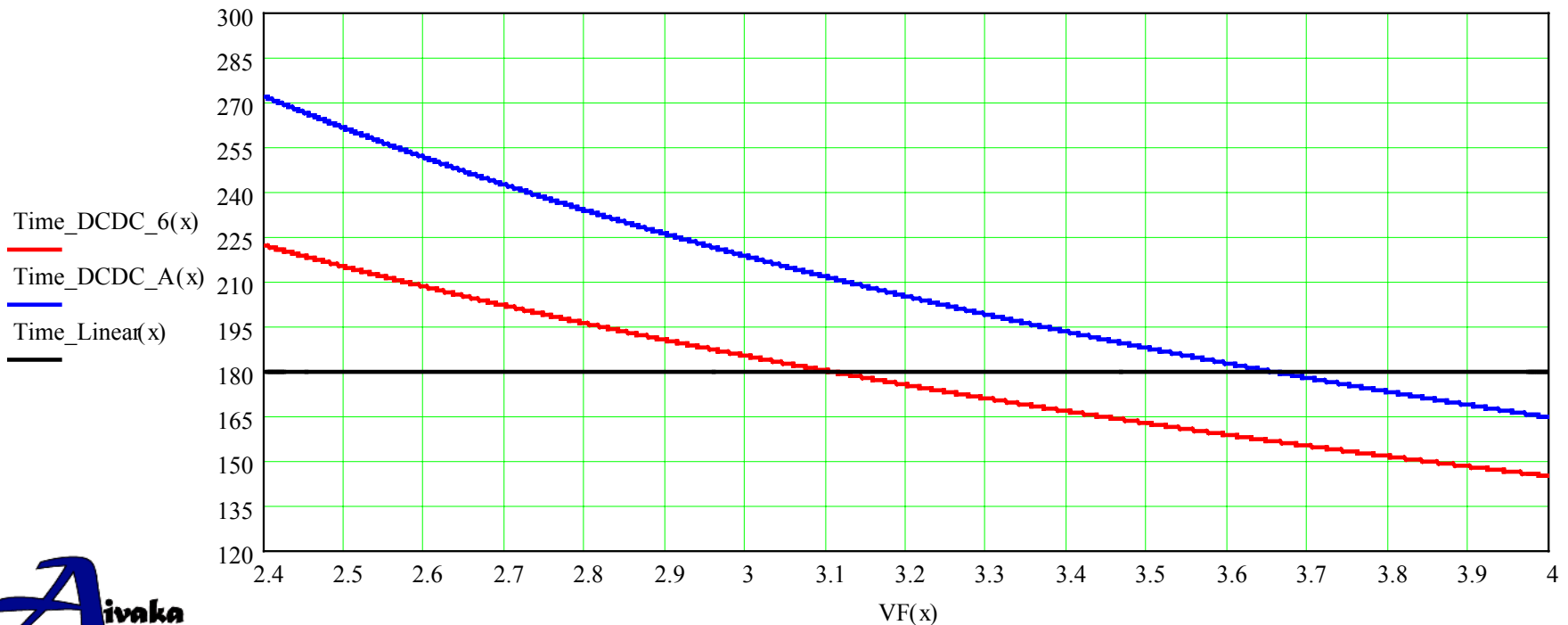Operating Time Vs. Forward Voltage VF(x) for 1050mAHr





**Saving The World One Battery
At A Time**

Advanced Technology & Customer Service